

Agenda

- How Driver Non-linear Range Affecting ADC system
- How Driver Noise Affecting ADC system
- SAR ADC Driver RC Optimization
- How Driver Bandwidth Affecting ADC system
- How Voltage Reference Affecting ADC system


Single Ended Input: ADC Input Range Considerations

PARAMETER ADS7042		TEST CONDITION	MIN	TYP	MAX	UNIT
ANALOG INPUT						
Full-scale input voltage span			0		AVDD	
Absolute Input voltage range	AINP to GND		0		AVDD+0.1	V
	AINM to GND		-0.1		+0.1	

Absolute Maximum Ratings

ADS7042	MIN	MAX	UNIT
AVDD to GND	-0.3	3.9	V
DVDD to GND	-0.3	3.9	V
AINP to GND	-0.3	AVDD + 0.3	V
AINM to GND	-0.3	+0.3	V

$AVDD+0.3 = 3.3V + 0.3V = 3.6V$

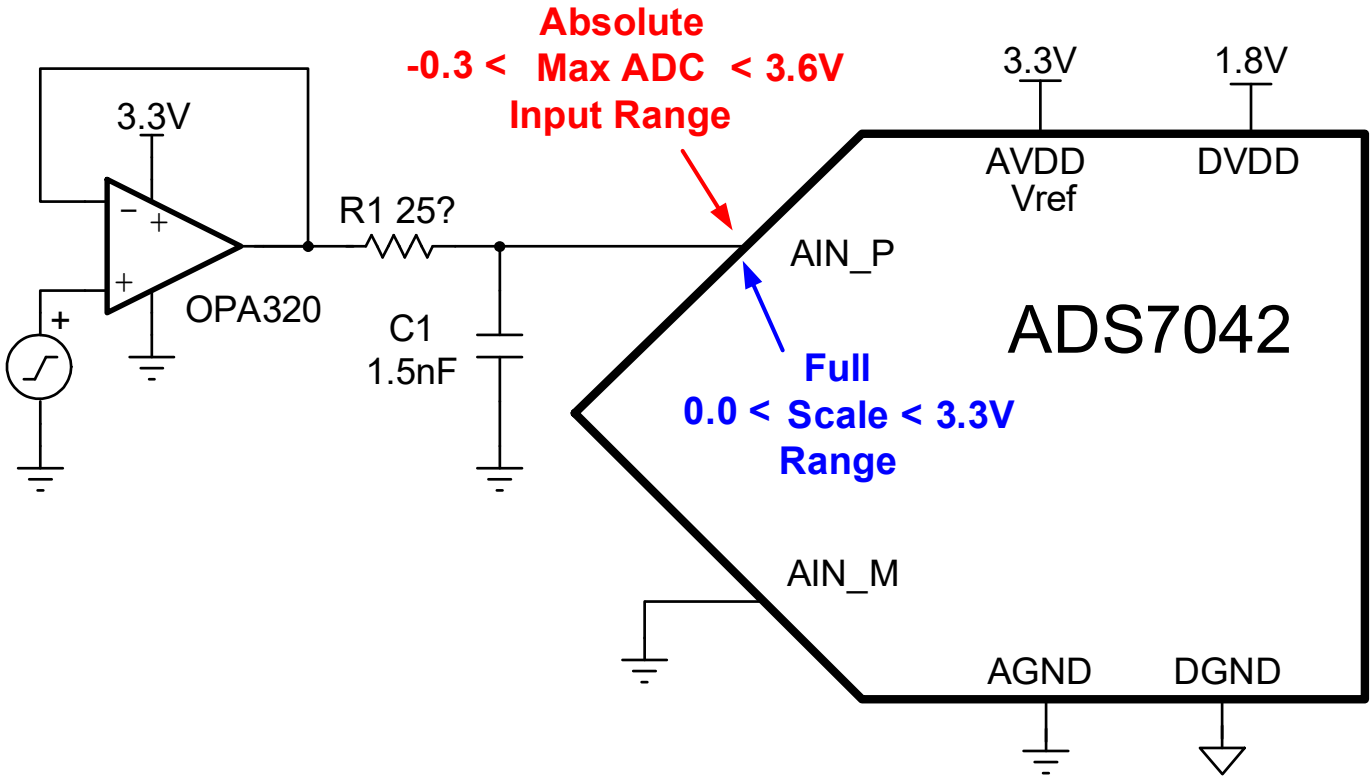

Single Ended Input: OPA320 Linear Range



PARAMETER OPA320		TEST CONDITION	MIN	TYP	MAX	UNIT
INPUT VOLTAGE						
Common-mode voltage range	V_{cm}		(V-) - 0.1		(V+)+0.1	V
OUTPUT						
Voltage swing from both rails	V_o	$R_L = 10k\Omega$		10	20	mV
		$R_L = 2k\Omega$		25	35	
OPEN-LOOP GAIN						
Open-loop gain	A_{OL}	$0.1 < V_o < (V+)-0.1V, R_L = 10k\Omega$	114	132		dB
		$0.2 < V_o < (V+)-0.2V, R_L = 2k\Omega$	108	123		

Amplifier Input Range	$-0.1V < V_{cm} < 3.4V$
Amplifier Output Range	$0.02 < V_o < 3.28V$
Amplifier Linear Range	$0.1 < V_o < 3.2V$
Worst Case Range	$0.1 < V_o < 3.2V$

Single Ended Input: Extending the Op Amp Range

Low Noise Negative Bias Generator

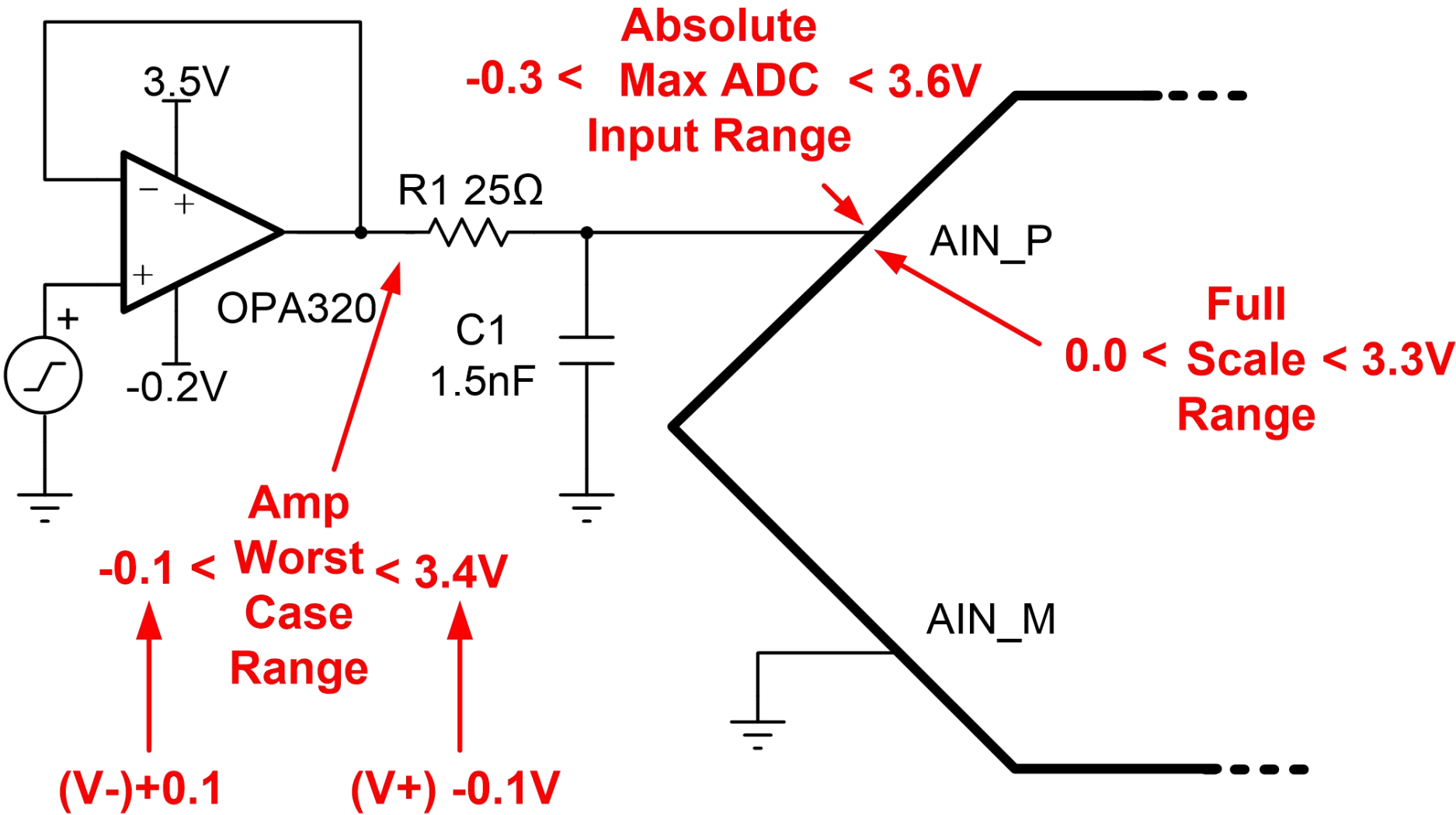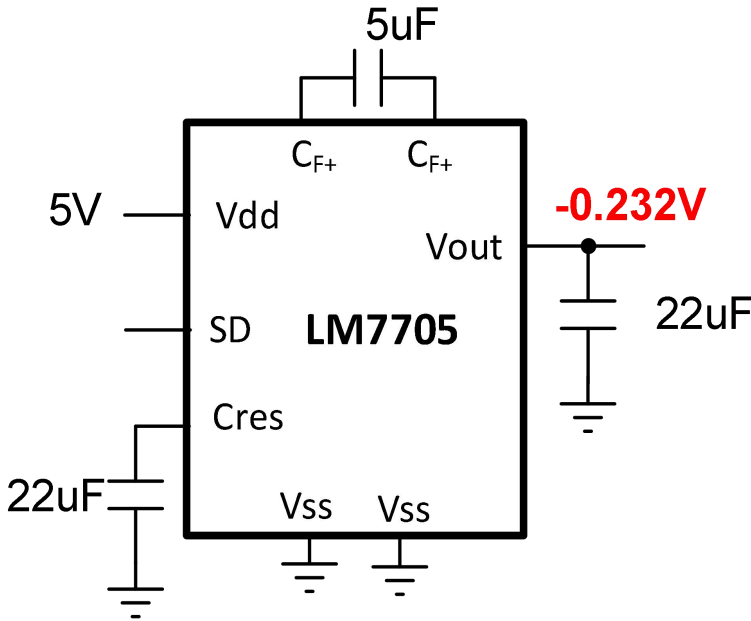- Regulated Output Voltage -0.232 V
- Output Voltage Tolerance 5%
- Output Voltage Ripple 4 mV_{PP}
- Maximum Output Current 26 mA



Single Ended Input: OPA625

PARAMETER OPA320		TEST CONDITION	MIN	TYP	MAX	UNIT
INPUT VOLTAGE						
Common-mode voltage range	V_{cm}		(V-)		(V+) - 1.15	V
OUTPUT						
Voltage swing from both rails	V_o	$R_L = 10k\Omega$		20	35	mV
		$R_L = 600\Omega$		60	80	
OPEN-LOOP GAIN						
Open-loop gain	A_{OL}	$0.15 < V_o < (V+) - 0.15V, R_L = 10k\Omega$	110	132		dB
		$0.2 < V_o < (V+) - 0.2V, R_L = 600\Omega$	106	128		

Amplifier input range	$0.0V < V_{cm} < 2.15V$
Amplifier output range	$0.035 < V_o < 3.265V$
Amplifier Linear Range	$0.15 < V_o < 3.15V$
Worst Case Range	$0.15 < V_o < 2.15V$



Inverting amplifier: Eliminate Common mode issue

PARAMETER OPA625		TEST CONDITION	MIN	TYP	MAX	UNIT
INPUT VOLTAGE						
Common-mode voltage range	V_{cm}		(V-)		(V+) - 1.15	V
OUTPUT						
Voltage swing from both rails	V_o	$R_L = 10k\Omega$		20	35	mV
		$R_L = 600\Omega$		60	80	
OPEN-LOOP GAIN						
Open-loop gain	A_{OL}	$0.15 < V_o < (V+) - 0.15V, R_L = 10k\Omega$	110	132		dB
		$0.2 < V_o < (V+) - 0.2V, R_L = 600\Omega$	106	128		

Amplifier input range	No Vcm limit
Amplifier output range	$0.035 < V_o < 3.265V$
Amplifier Linear Range	$0.15 < V_o < 3.15V$
Worst Case Range	$0.15 < V_o < 3.15V$

Input Crossover Distortion in Rail-to-Rail Inputs



PARAMETER OPA316		TEST CONDITIONS	MIN	TYP	MAX	UNIT
INPUT VOLTAGE RANGE						
V_{CM}	Common mode voltage range	$T_A = -40^{\circ}\text{C}$ to 85°C	-0.2		$(V^+)+0.1$	V
CMRR	Common mode Rejection	$V_s = 5\text{V}$, $-0.1\text{V} < V_{cm} < 3.6\text{V}$	76	90		dB
		$V_s = 5\text{V}$, $-0.1\text{V} < V_{cm} < 5.2\text{V}$	65	80		dB

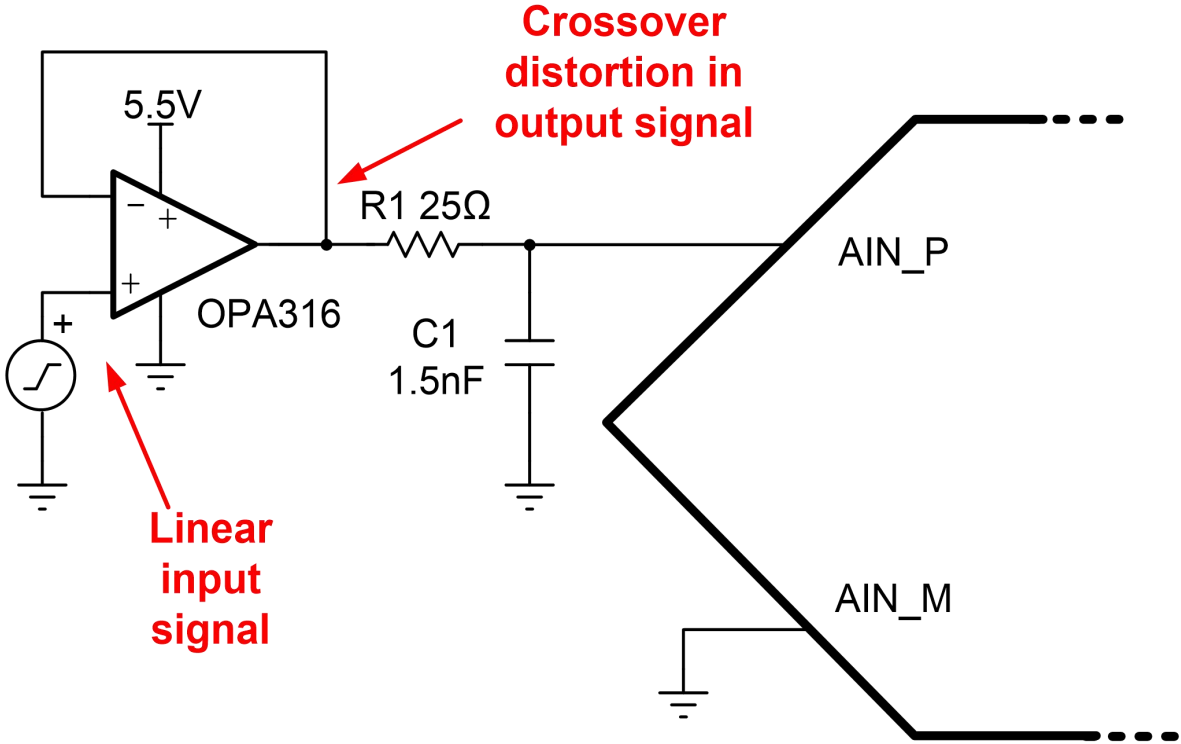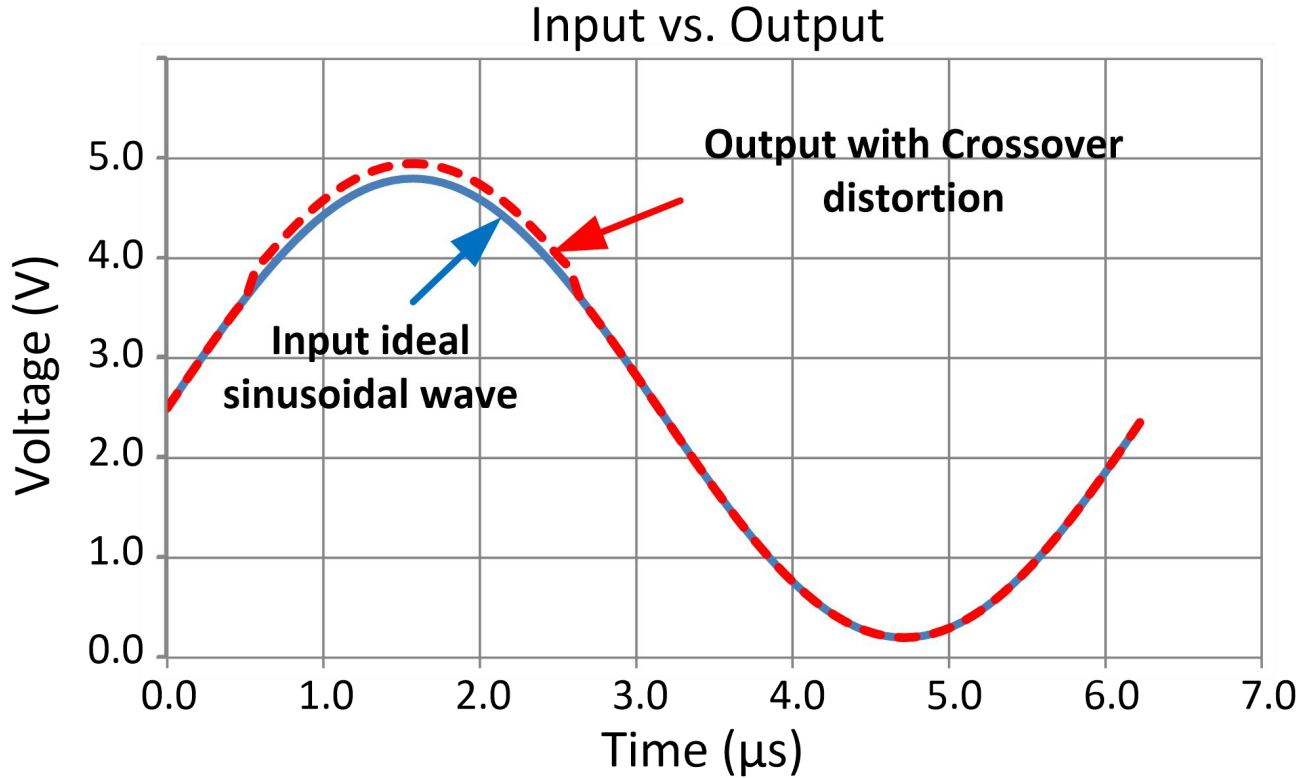


Input Cross-Over distortion vs Zero Cross-Over

PARAMETER: OPA350 – Has Crossover		MIN	TYP	MAX	UNIT
INPUT VOLTAGE RANGE					
V_{CM}	Common mode voltage range	$(V_-)-0.1$		$(V_+)+0.1$	V
CMRR	Common mode Rejection $-0.1V < V_{cm} < 5.6V$	74	90		dB


PARAMETER: OPA320 – Zero Cross-Over		MIN	TYP	MAX	UNIT
INPUT VOLTAGE RANGE					
V_{CM}	Common mode voltage range	$(V_-)-0.1$		$(V_+)+0.1$	V
CMRR	Common mode Rejection $-0.1V < V_{cm} < 5.6V$	100	114		dB

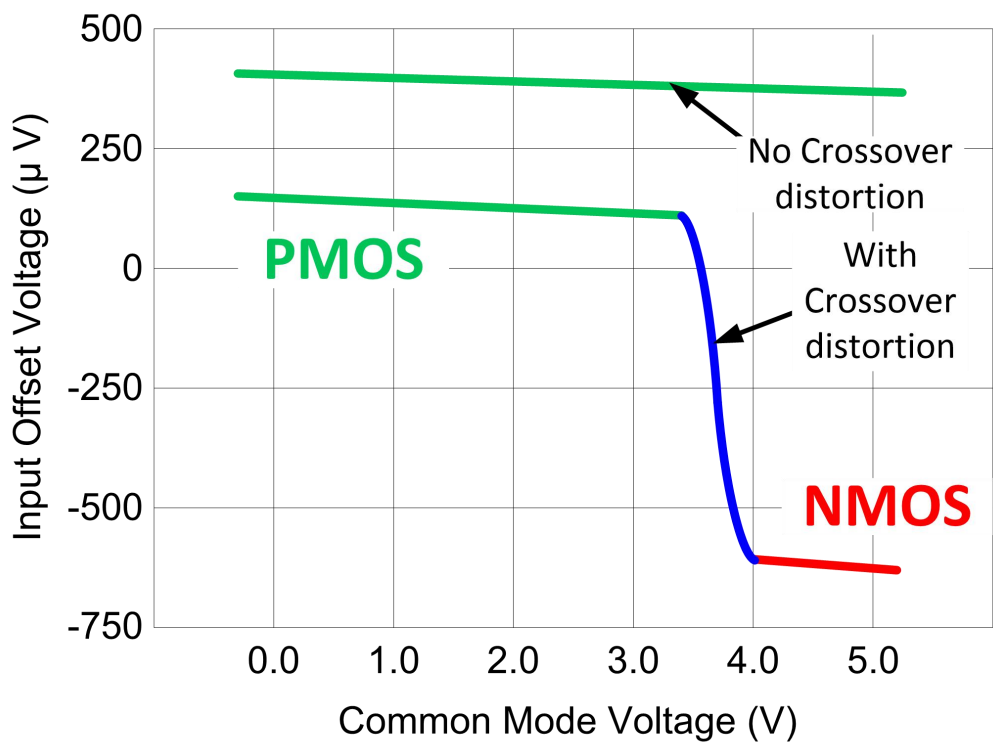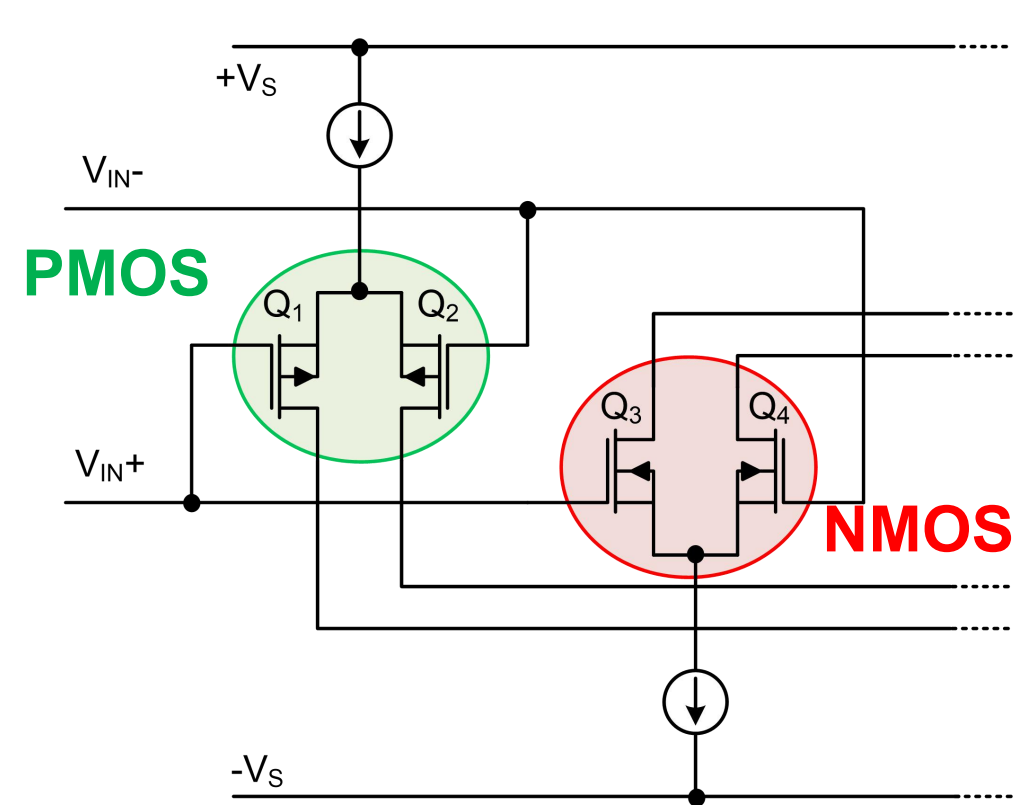

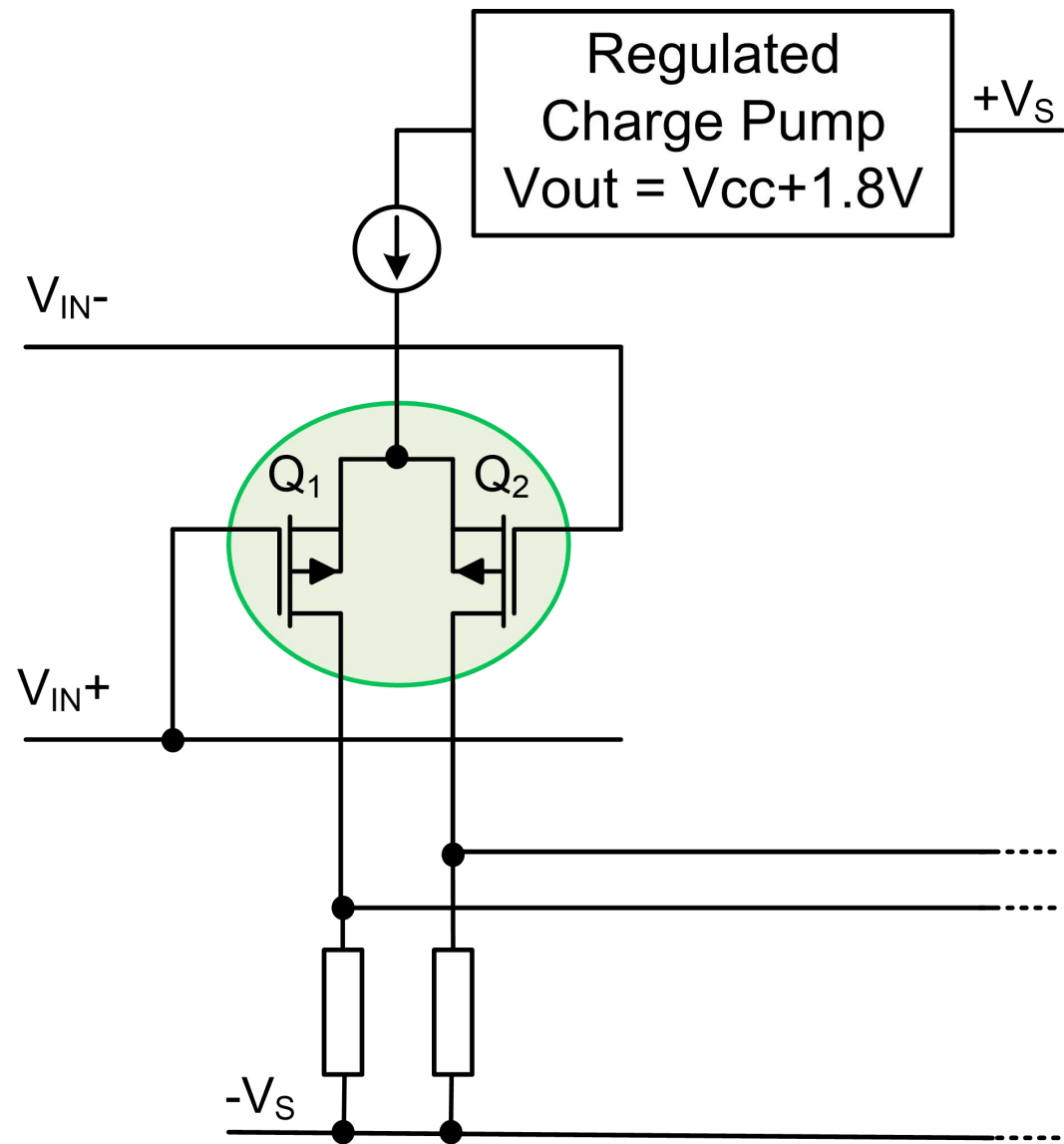Optimize bypass for internal charge pump op amps



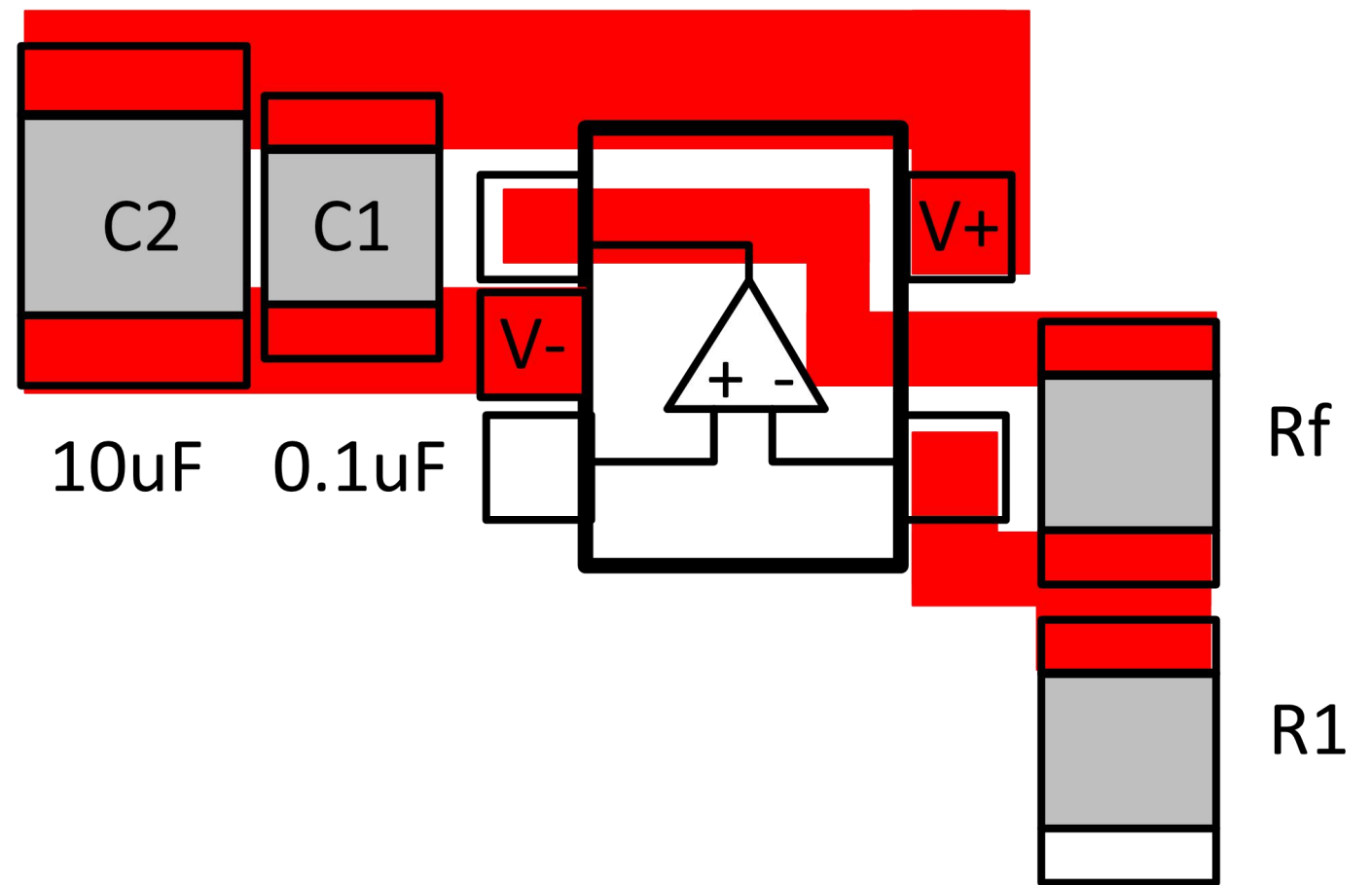Short direct connections from supply to decoupling



Finding standard


quick quiz.

Quiz: Linear Range ADC + OPA</

Quiz: Linear Range ADC + OPA</

Quiz: Linear Range ADC + OPA

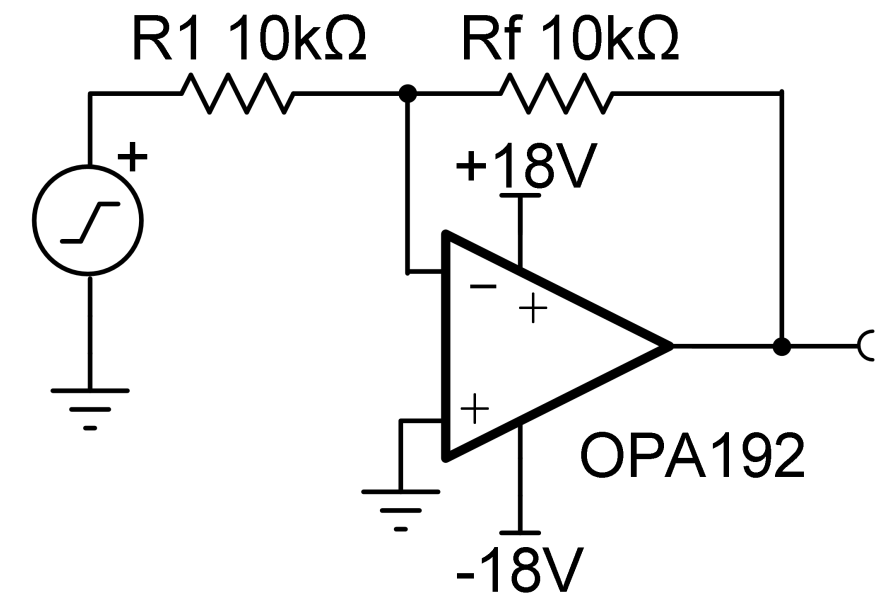6. Which of the following applies to an inverting amplifier topology.
- a. Gain error is determined by resistor tolerance.
 - b. The input impedance is relatively low ($10\text{k}\Omega$ in this case).
 - c. The circuit will not have crossover distortion issues.
 - d. The output will be loaded by the feedback network ($10\text{k}\Omega$ in this case).
 - e. All the statements apply to the inverting topology.
 - f. None of the statements apply to the inverting topology.



Op Amp

Demo – Driver Crossover

<

SNR of Ampl

SNR

quick quiz.

Quiz: Calcul

Demo – Driver Noise Difference

<

